

Sottrattore combinatorio e sequenziale

lunedì 3 gennaio 2022 11:02

COMBINATORIO

SOURCE CODE

```
library IEEE;
use IEEE.std_logic_1164.all;

entity Subtracter is
    generic(nb := integer := 16);
    port ( A : in std_logic_vector (nb-1 downto 0);
           B : in std_logic_vector (nb-1 downto 0);
           sub : out std_logic_vector (nb downto 0));
end Subtracter;

architecture Behav of Subtracter is
begin
    begin
        -- A-B = A + not B + 1
        c(0) <= '1';
        p <= (A(nb-1) xor not B(nb-1)) & (A xor not B);
        g <= (A(nb-1) and not B(nb-1)) & (A and not B);
        c(nb+1 downto 1) <= g or (p and c(nb downto 0));
        sub <= p xor c(nb downto 0);
    end behav;
```

TESTBENCH

```
entity SimSub is
    generic(nb := integer := 16);
end SimSub;

architecture Behav of SimSub is
component Subtracter is
    generic(nb := integer := 16);
    port ( A : in std_logic_vector (nb-1 downto 0);
           B : in std_logic_vector (nb-1 downto 0);
           sub : out std_logic_vector (nb downto 0));
end component;
signal IA, IB : std_logic_vector(nb-1 downto 0);
signal Osub : out std_logic_vector(nb downto 0);

begin
    begin
        CUT: subtracter port map(IA, IB, Osub);
        process
        begin
            for va in -(2**nb) to (2**nb)-1 loop
                for vb in -(2**nb) to (2**nb)-1 loop
                    IA <= conv_std_logic_vector(va,nb);
                    IB <= conv_std_logic_vector(vb,nb);
                    wait for 10 ns;
                end loop;
            end loop;
        end process;
    end Behav;
```

Questo circuito, se simulato, solleva un errore di temperatura di giunzione superata a causa dell'alta dissipazione di potenza per via della natura combinatoria.

SEQUENZIALE

SOURCE CODE

```
library IEEE;
use IEEE.std_logic_1164.all;

entity Subtracter is
    generic(nb := integer := 16);
    port ( A : in std_logic_vector (nb-1 downto 0);
           B : in std_logic_vector (nb-1 downto 0);
           clk : in std_logic;
           sub : out std_logic_vector (nb downto 0));
end Subtracter;
```

```

architecture Behav of Subtracter is
signal p, g : std_logic_vector (nb downto 0);
signal c : std_logic_vector (nb+1 downto 0);
signal IA, IB : in std_logic_vector (nb-1 downto 0); è segnale in uscita
signal Osub : out std_logic_vector (nb downto 0); dati registrati
begin
    begin
        -- A-B = A + not B + 1
        c(0) <= '1'; → 1 inizializza da sommare
        p <= ( IA(nb-1) xor not IB(nb-1) ) & ( IA xor not IB );
        g <= ( IA(nb-1) and not IB(nb-1) ) & ( IA and not IB );
        c(nb+1 downto 1) <= g or (p and c(nb downto 0));
        Osub <= p xor c(nb downto 0);
    process
        if rising_edge( clk ) then
            IA <= A;
            IB <= B;
            sub <= Osub;
        end if;
    end process;
end behav;

```

TESTBENCH

```

entity SimSub is
    generic (nb := integer := 16);
end SimSub;


architecture Behav of SimSub is
component Subtracter is
    generic(nb := integer := 16);
    port ( A : in std_logic_vector (nb-1 downto 0);
           B : in std_logic_vector (nb-1 downto 0);
           clk : in std_logic;
           sub : out std_logic_vector (nb downto 0);
    end component;
    signal IA, IB : std_logic_vector(nb-1 downto 0);
    signal Osub : out std_logic_vector(nb downto 0);
    signal Iclk : std_logic := '0';
    -- constant Tclk : time:= 5 ns; COMMENTATO

begin
    begin
        CUT: subtracter port map(IA, IB, Osub);

        process
        begin
            wait for Tclk+100 ns; → sincronizzo col ritardo del clock
            for va in -(2**nb-1) to (2**nb-1)-1 loop
                for vb in -(2**nb-1) to (2**nb-1)-1 loop
                    IA <= conv_std_logic_vector(va,nb);
                    IB <= conv_std_logic_vector(vb,nb);
                    wait for 10 ns;
                end loop;
            end loop;
        end process;

        process → periodo del clock
        begin
            wait for 5 ns;
            -- potrei scriverlo anche come costante constant Tclk : time:= 5 ns;
            Iclk <= not Iclk;
        end process;
    end Behav;

```

 

disallineamento / latenza

del circuito

ottengo il primo risultato
in uscita con del ritardo

Route report timing summary

| Design Timing Summary
| -----

| WNS(ns) | TNS(ns) | TNS Failing Endpoints | TNS Total Endpoints | WHS(ns) | THS(ns) | THS Failing Endpoints | THS Total Endpoints |
|---------|---------|-----------------------|---------------------|---------|---------|-----------------------|---------------------|
| 0.341 | 0.000 | 0 | 17 | 0.198 | 0.000 | 0 | 0 |

↳ essendo > 0 vuol dire che posso funzionare con un periodo maggiore di clock

All user specified timing constraints are met.