

Codici da sapere

giovedì 6 gennaio 2022

11:22

FULL ADDER

entity FA is

generic (n : integer);

port(

A, B, Cin : in bit;

S, Cout : out bit);

end FA;

architecture ex1 of FA is

signal p,g : bit

begin

p <= A xor B;

g <= A and B;

Cout <= (p and Cin) or g;

S <= p xor Cin;

end ex1;

CARRY LOOK AHEAD senza overflow

entity RC is

generic (n : integer);

port(

A, B : in std_logic_vector(n-1 downto 0);

S: out std_logic_vector(n downto 0);

Cin : in std_logic;

end RC;

architecture ex1 of RC is

signal p,g : std_logic_vector(n-1 downto 0);

signal carry: std_logic_vector(n downto 0);

begin

p <= A xor B;

g <= A and B;

carry(0) <= Cin;

carry(n downto 1) <= p and carry(n-1 downto 0) or g;

S <= p xor carry(n-1 downto 0);

end ex1;

CARRY LOOK AHEAD con segno

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RC is
    generic (n : integer);
    port(
        A, B: in std_logic_vector(n-1 downto 0); -- 8bit
        S: out std_logic_vector(n downto 0); --9 bit
        Cin : in std_logic);
end RC;

architecture ex1 of RC is
    signal p,g : std_logic_vector(n downto 0);
    signal carry: std_logic_vector(n+1 downto 0); -- 10 bit

    begin
        p <= (A(n-1) xor B(n-1)) & (A xor B); -- 9 bit
        g <= (A(n-1) and B(n-1)) & (A and B); -- 9 bit

        carry(0) <= Cin;
        carry(n+1 downto 1) <= (p and carry(n downto 0)) or g;

        S <= p xor carry(n downto 0);

    end ex1;
```

FLIP FLOP con clear e reset asincroni sensibile ai fronti di salita del clock

```
entity FF is
    generic (n:integer);
    port (
        D: in std_logic_vector(n-1 downto 0);
        pr: in std_logic;
        clr: in std_logic;
        clk: in std_logic;
        R: in std_logic_vector(n-1 downto 0)mm
    );
end FF;

architecture Behav of FF is

    begin

        process(clk, pr, clr)
```

```

        if (clr = '1') then
            R <= (others => '0');
        elsif (pr = '1') then
            R <= (others => '1');
        else if (rising_edge(clk)) then
            R <= D;
        end process;
end Behav;

```

FLIP FLOP con clear e reset sincroni sensibile ai fronti di salita del clock

```

entity FF is
    generic (n:integer);
    port (
        D: in std_logic_vector(n-1 downto 0);
        pr: in std_logic;
        clr: in std_logic;
        clk: in std_logic;
        R: in std_logic_vector(n-1 downto 0)
    );
end FF;

```

architecture Behav of FF is

```

begin

    process(clk)
        if (rising_edge(clk))
            if (clr = '1') then
                R <= (others => '0');
            elsif (pr = '1') then
                R <= (others => '1');
            elsif (pr = '0' and clr = '0') then
                R <= D;
            end process;
        end process;
end Behav;

```

SOTTRATTORE

```

library IEEE;
use IEEE.std_logic_1164.all;

```

```

entity sub is
    generic (n:integer)
    port(

```



```

        A, B : in std_logic_vector(n-1 downto 0);
        sel: in std_logic;
        Ris: out std_logic_vector(n downto 0);
    );
end sub;

architecture behav of sub is
    signal EA, EB, nB, p, g: std_logic_vector(n downto 0);
    signal carry: std_logic_vector(n+1 downto 0);

begin
    EA <= A(n-1) & A;
    nB <= B(n-1) & B;
    EB <= nB when sel='0' else
        not nB when sel='1' else
        (others => 'x');
    carry(0) <= sel;
    carry(n+1 downto 1) <= (p and carry(n downto 0)) or g;
    p <= EA xor EB;
    g <= EA and EB;
    Ris <= p xor carry(n downto 0);

end behav;

```

PACKAGE

```


library IEEE;
use IEEE.std_logic_1164.all;

package costanti is
    constant n: integer := 8;
end package costanti;


```




INVERTER

 


NAND

 


AND

 

NOR

 

OR

 

XNOR

